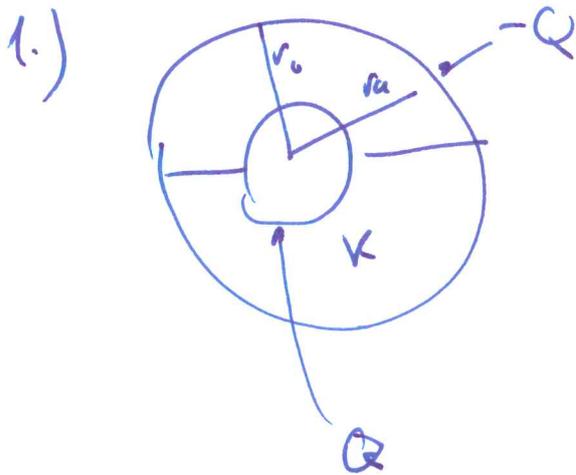


Problem Set 7: Solutions

①



2.) capacitance without dielectric:

$$C = \frac{Q}{V_{ab}} \quad V_{ab} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_a} - \frac{1}{r_b} \right)$$

$$C = 4\pi\epsilon_0 \left(\frac{r_a r_b}{r_b - r_a} \right)$$


capacitance with dielectric:

$$C = \frac{Q}{V_{ab}} \quad V_{ab} = \frac{Q}{4\pi\epsilon} \left(\frac{1}{r_a} - \frac{1}{r_b} \right)$$

$$C = 4\pi\epsilon_0 K \frac{r_a r_b}{r_b - r_a} =$$

half-filled $\Rightarrow C = \frac{4\pi\epsilon_0 r_a r_b}{(r_b - r_a)} \left(\frac{1+K}{2} \right)$

b.)

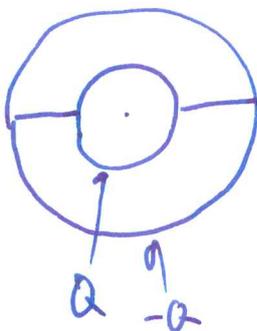

e-field: Q divides on surface so that overall σ is constant

$$\sigma_i = \left(1 - \frac{1}{K} \right) \sigma$$

upper half $\Rightarrow \sigma$

Count upper half: σ (only free charges)
 lower half: σ (free + bound charges)

(2)

$$\sigma_{\text{free}}^{\text{upper}} = \sigma_{\text{free}}^{\text{lower}} + \sigma_i^{\text{lower}}$$

$$\sigma_i^{\text{lower}} = \left(1 - \frac{1}{\kappa}\right) \sigma_{\text{free}}^{\text{lower}}$$

$$\sigma_{\text{free}}^{\text{upper}} = \frac{\sigma_{\text{free}}^{\text{lower}}}{\kappa} - \left(\kappa - \frac{1}{\kappa}\right) \sigma_{\text{free}}^{\text{lower}} = \frac{\sigma_{\text{free}}^{\text{lower}}}{\kappa}$$

$$\sigma_{\text{free}}^{\text{upper}} + \sigma_{\text{free}}^{\text{lower}} = \sigma = \frac{Q}{4\pi\epsilon_0 r_a^2}$$

$$\sigma_{\text{free}}^{\text{upper}} + \kappa \sigma_{\text{free}}^{\text{upper}} = \sigma_{\text{free}}^{\text{upper}} \left(1 + \frac{1}{\kappa}\right) = \sigma = \frac{3Q}{4\pi\epsilon_0 r_a^2}$$

$$\sigma_{\text{free}}^{\text{upper}} = \frac{3Q}{4\pi\epsilon_0 r_a^2} \frac{\kappa}{\kappa+1}$$

$$Q' = \frac{Q}{\kappa+1}$$

electric field: $E(r) = \frac{Q}{4\pi\epsilon_0 r^2 (\kappa+1)}$

c.)
$$\sigma_{\text{free}}^{\text{upper}} = \frac{3Q}{4\pi\epsilon_0 r_a^2} \frac{1}{(\kappa+1)}$$


$$\sigma_{\text{free}}^{\text{lower}} = \frac{3Q}{4\pi\epsilon_0 r_a^2} \frac{\kappa}{(\kappa+1)}$$

d.) inner surface:
$$\sigma_i = \left(1 - \frac{1}{\kappa}\right) \frac{3Q}{4\pi\epsilon_0 r_a^2} \frac{\kappa}{(\kappa+1)}$$

outer surface:
$$\sigma_i = \left(1 - \frac{1}{\kappa}\right) \frac{3Q}{4\pi\epsilon_0 r_b^2} \frac{\kappa}{\kappa+1}$$

e) zero: \vec{E} -field is parallel to the surface, 3
 so it will not polarize in the direction perpendicular to the surface

2.)

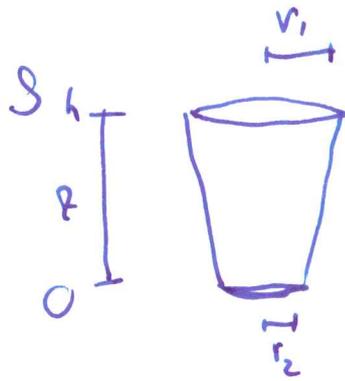


thin slice: 
 $A = \pi r^2$ r depends on z
 $r = r(z)$
 $R = \frac{\rho dz}{A} = \frac{\rho dz}{\pi r(z)^2}$

$$r(z) = \left(\frac{r_1 - r_2}{h}\right)z + r_2 = Az + r_2 \quad A = \frac{r_1 - r_2}{h}$$


$$R = \int_0^h \frac{\rho dz}{\pi (Az + r_2)^2} = \frac{\rho}{\pi} \left(-\frac{1}{Az + r_2} \right) \Big|_0^h$$

$$= \frac{\rho}{\pi} \left[\frac{1}{r_2} - \frac{1}{r_1} \right]$$

3.)

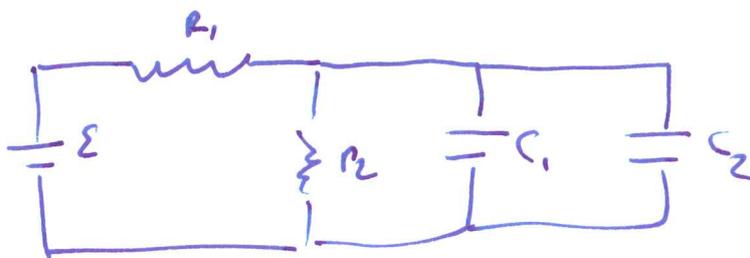

↓ parallel capacitor

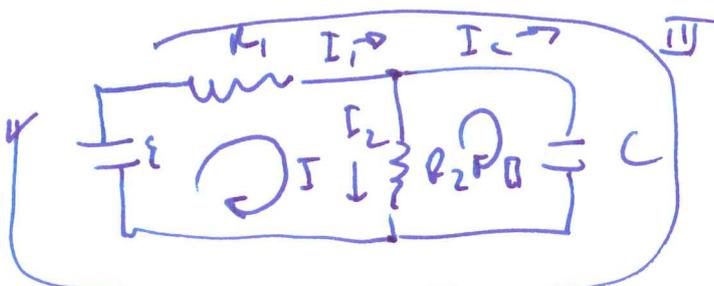

$$C = C_1 + C_2$$

Kirchhoff: $I_1 = I_2 + I_C$

I) $\varepsilon - I_1 R_1 - I_2 R_2 = 0$

II) ~~$-\varepsilon + I_2 R_2 = 0$~~ $-\frac{Q}{C} + I_2 R_2 = 0$

III) $\varepsilon - I_1 R_1 - \frac{Q}{C} = 0$

~~from~~ from III: and from junction rule:

$$\varepsilon - I_1 R_1 - \frac{Q}{C} = 0 \rightarrow \varepsilon - I_2 R_1 - I_c R_1 - \frac{Q}{C} = 0 \quad (4)$$

$$\text{from II: } -\frac{Q}{C} + I_2 R_2 = 0 \Rightarrow I_2 = +\frac{Q}{R_2 C}$$

$$\varepsilon - \frac{Q R_1}{C R_2} - I_c R_1 - \frac{Q}{C} = 0$$

$$\varepsilon - \frac{Q}{C} \left(\frac{R_1}{R_2} + 1 \right) - I_c R_1 = 0$$

$$\text{define } C' = \frac{C R_2}{R_2 + R_1}$$

$$\varepsilon - \frac{Q}{C'} - I_c R_1 = 0 \quad I_c = \frac{dQ}{dt}$$

$$\varepsilon - \frac{Q}{C'} - \frac{dQ}{dt} R_1 = 0$$

$$\varepsilon C' - Q - \frac{dQ}{dt} R_1 C' = 0$$

$$-\frac{dQ}{dt} R_1 C' = Q - \varepsilon C'$$

$$\frac{dQ}{Q - \varepsilon C'} = -\frac{dt}{R_1 C'}$$

$$\ln \left(\frac{Q(t) - \varepsilon C'}{Q(0) - \varepsilon C'} \right) = -t / R_1 C'$$

\Rightarrow final charge on combined capacitor

$$Q(\infty) = \varepsilon C'$$

$$Q(\infty) = \frac{\varepsilon C R_2}{R_2 + R_1} = \frac{\varepsilon (C_1 + C_2) R_2}{R_2 + R_1}$$

(5)

Q_1 - charge on capacitor 1

$$Q_1 = \frac{Q}{1 + \frac{C_1}{C_2}} \quad Q_2 = \frac{Q}{1 + \frac{C_2}{C_1}}$$

$$Q_1 = 18 \mu\text{C} \Rightarrow$$

$$18 \times 10^{-6} \text{C} = \frac{Q}{1 + \frac{3}{6}} = \frac{2Q}{3}$$

$$\frac{3}{2} \times 18 \mu\text{C} = Q \quad Q = 27 \mu\text{C}$$

$$Q_2 = \frac{27 \mu\text{C}}{1 + \frac{6}{3}} = 9 \mu\text{C}$$

b.) $R_2 = ?$

$$Q(\infty) = \frac{\varepsilon (C_1 + C_2) R_2}{R_2 + R_1}$$

$$(27 \mu\text{C}) = \frac{(60.0 \text{V})(9.00 \mu\text{F})(2.00 \Omega)}{(2.00 \Omega + R_1)}$$

$$(2.00 \Omega + R_1) = \frac{(60.0)(9.00)(2.00)}{27}$$

$$2 + R_1 = 20.2 = 40$$

$$R_1 = 38 \Omega$$

28.87

(6)


$$g(x) = g_0 e^{-x/L}$$

$$E = gJ$$

$$V = Ed = gJd$$

$$= \frac{gJd}{t} \Rightarrow R = \frac{sd}{A}$$

a.)

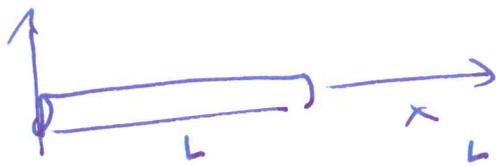

total resistance: $R = \frac{g_0}{A} \int_0^L e^{-x/L} dx$

$$R = \frac{g_0}{A} e^{-x/L} (-L) \Big|_0^L = \frac{g_0 L}{A} (1 - e^{-1})$$

current $\Rightarrow I = \frac{V}{R} = \frac{VA}{\frac{g_0 L}{A} (1 - \frac{1}{e})}$

b.)

$$J = \frac{I}{A} = \frac{V}{g_0 L (1 - \frac{1}{e})}$$

$$g(x) = g_0 e^{-x/L}$$

$$\Rightarrow E(x) = g(x)J = \frac{V}{g_0 L (1 - \frac{1}{e})} e^{-x/L}$$

c.)

$$V(x) = -\int_0^x dx' E(x')$$



$$= -\int_0^x dx' \frac{V e^{-x'/L}}{L(1 - \frac{1}{e})} = \frac{-V}{L(1 - \frac{1}{e})} \int_0^x dx' e^{-x'/L}$$

$$= \frac{+V}{L(1 - \frac{1}{e})} e^{-x'/L} (+L) \Big|_0^x$$


$$= \frac{V}{1 - \frac{1}{e}} (1 - e^{-x/L})$$

d.)


$$g(x)$$

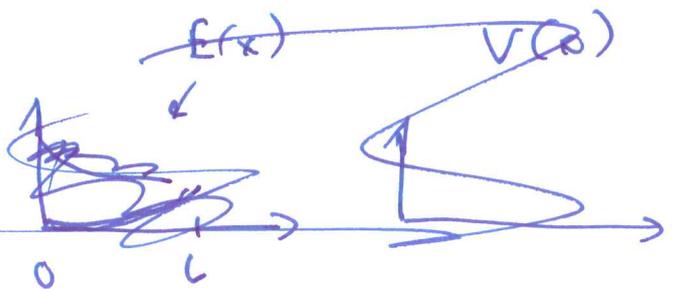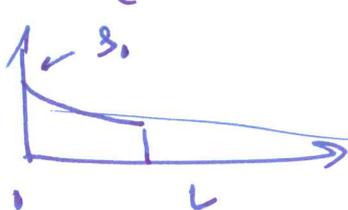


d.) $\beta(x)$

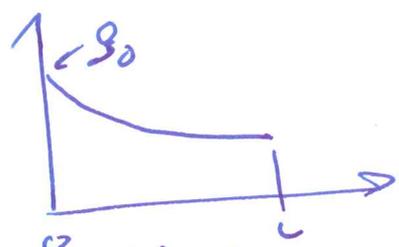

$E(x)$

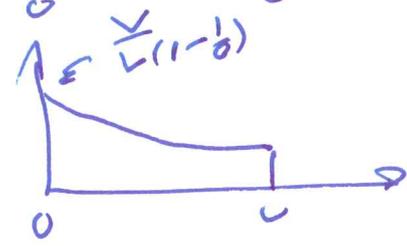


$v(x)$

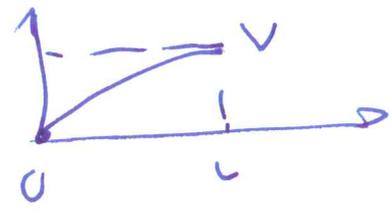


5. 26.61

(a)

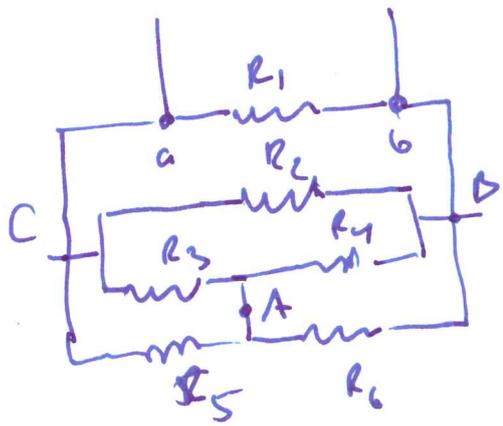


- $R_1 = 100.0 \Omega$
- $R_2 = 50.0 \Omega$
- $R_3 = 75.0 \Omega$
- $R_4 = 25.0 \Omega$
- $R_5 = 40.0 \Omega$
- $R_6 = 50.0 \Omega$

equivalent to

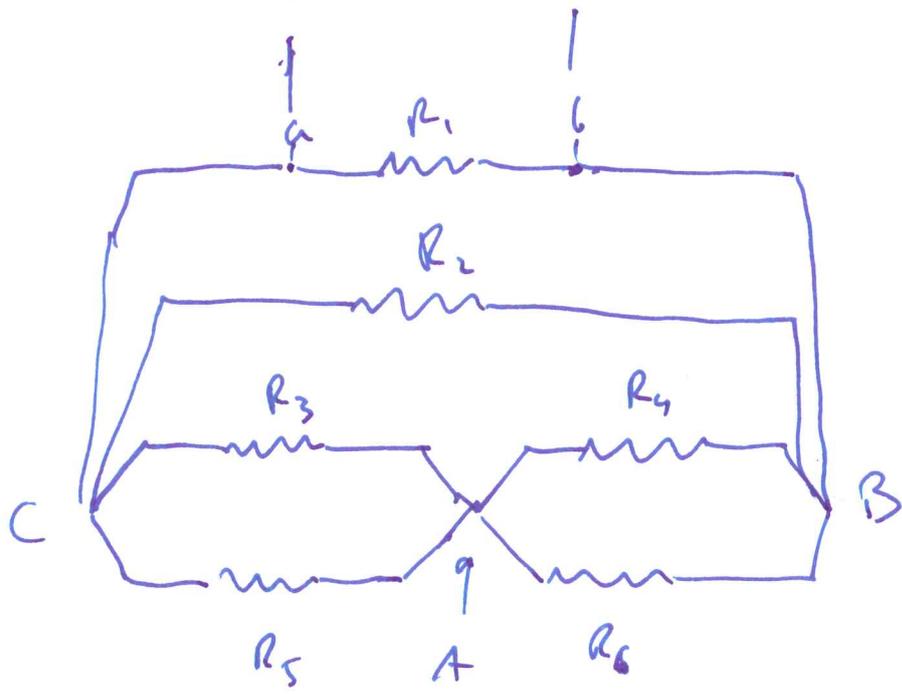


8

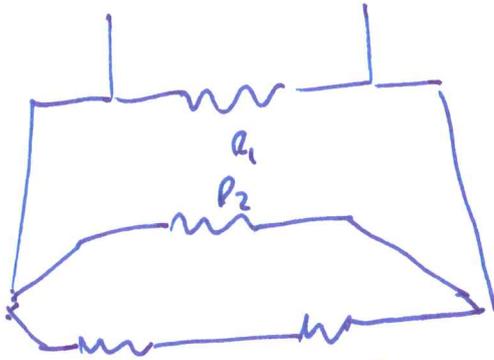


$$\frac{R_3 R_5}{R_3 + R_5} \quad \frac{R_4 R_6}{R_4 + R_6} \rightarrow 26.1 \Omega, 16.7 \Omega$$

↓

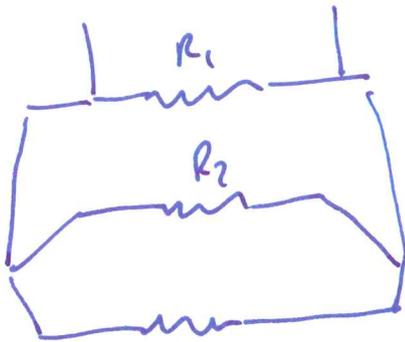

$$\frac{R_3 R_5}{R_3 + R_5} + \frac{R_4 R_6}{R_4 + R_6} = R' = 47.8 \Omega$$


↓

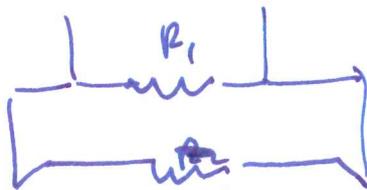

$$\frac{R_2 R'}{R_1 + R'} = R'' = 23.1$$

Equivalent resistance: $\frac{R'' R_1}{R_1 + R''} = 18.7 \Omega$



(6)

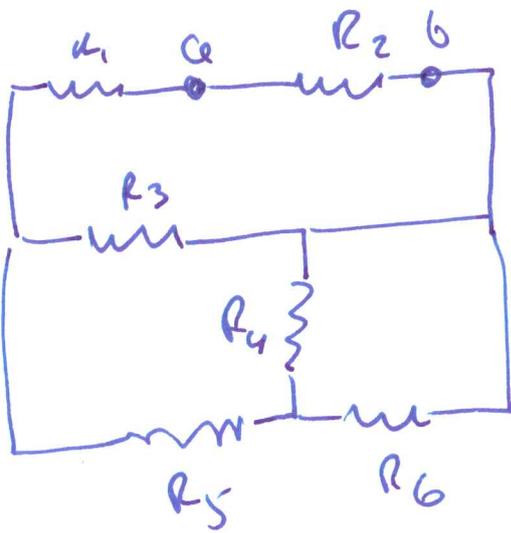


(9)

- $R_1 = 17.00 \Omega$
- $R_2 = 10.00 \Omega$
- $R_3 = 60.00 \Omega$
- $R_4 = 30.00 \Omega$
- $R_5 = 20.0 \Omega$
- $R_6 = 45.0 \Omega$

re draw

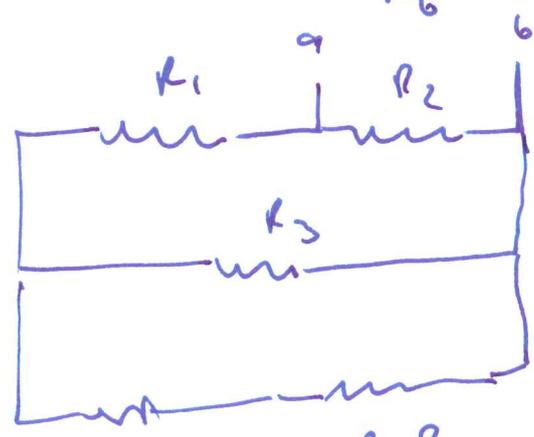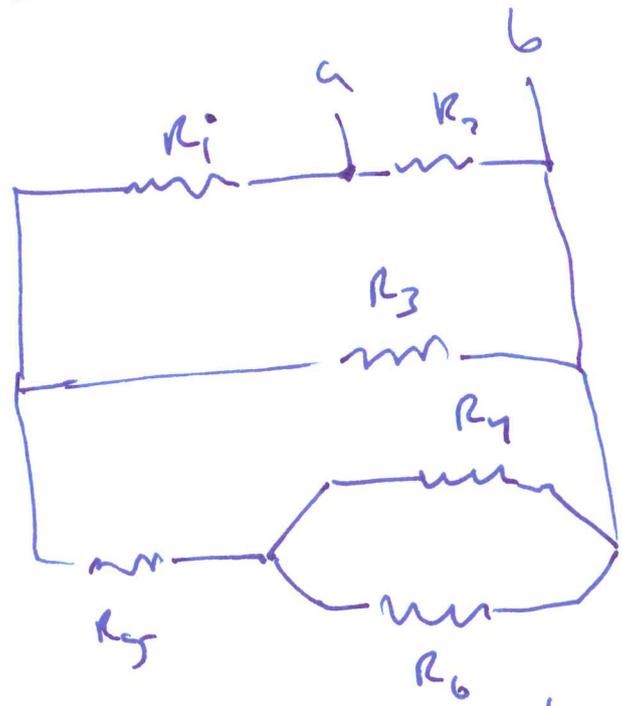

→

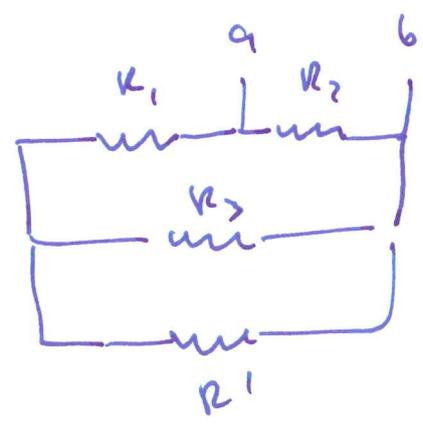

$$R_5 + \frac{R_4 R_6}{R_4 + R_6}$$

↓


$$18 \Omega$$

$$R' = R_5 + \frac{R_4 R_6}{R_4 + R_6}$$

$$R' = 38.0 \Omega$$



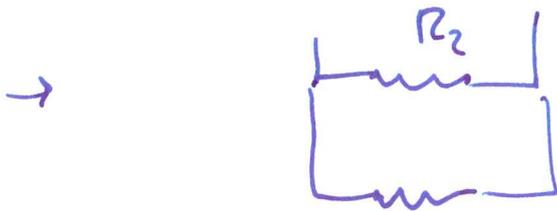
$$R'' = \frac{R_2 R_3}{R_2 + R_3} = 23.3 \Omega$$



$$R''' = R'' + R_1 = 30.3 \Omega$$

equivalent resistance $\frac{R_2 R'''}{R_2 + R'''} = 17.5 \Omega$

6.) 26.66

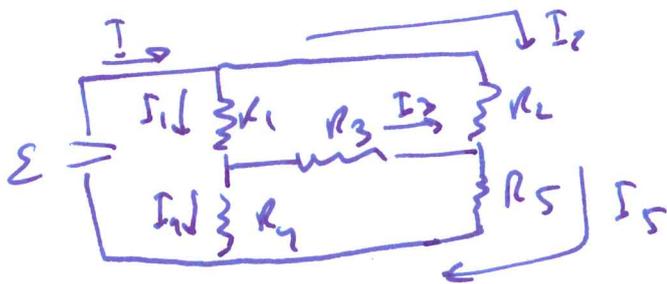

- $R_1 = 1.00 \Omega$
- $R_2 = 2.00 \Omega$
- $R_3 = 1.00 \Omega$
- $R_4 = 2.00 \Omega$
- $R_5 = 1.00 \Omega$

$$E = 14.0 \text{ V}$$

Kirchhoff:

$$I = I_1 + I_2$$

$$I_1 = I_3 + I_4$$

$$I_2 + I_3 = I_5$$

$$I_4 + I_5 = I$$

Loop 1: $E - I_1 R_1 - I_4 R_4 = 0$

Loop 2: $E - I_2 R_2 - I_5 R_5 = 0$

Loop 3: $-I_2 R_2 + I_3 R_3 + I_1 R_1 = 0$

Loop 4: $-I_3 R_3 - I_5 R_5 + I_4 R_4 = 0$

~~$-I_2 R_2 - I_5 R_5 + I_4 R_4 + I_1 R_1 = 0$~~ $E - I_1 R_1 - I_3 R_3 - I_5 R_5 = 0$

(11)

$$\Sigma - I_1 R_1 - (I_1 - I_3) R_4 = 0$$

$$\Sigma - I_1 (R_1 + R_4) + I_3 R_4 = 0$$

$$\Sigma - I_2 R_2 - I_2 R_5 - I_3 R_5 = 0$$

$$\Sigma - I_2 (R_2 + R_5) - I_3 R_5 = 0$$

$$\Sigma - I_1 (R_1 + R_4) + I_3 R_4 = 0$$

$$\Sigma - I_2 (R_2 + R_5) - I_3 R_5 = 0$$

$$I_2 = \frac{I_1 R_1 + I_3 R_3}{R_2}$$

$$\Sigma - I_1 (R_1 + R_4) + I_3 R_4 = 0$$

$$\Sigma - I_1 \frac{R_1}{R_2} (R_2 + R_5) - \frac{I_3 R_3}{R_2} (R_2 + R_5) - I_3 R_5 = 0$$

$$\Sigma - I_1 \frac{R_1}{R_2} (R_2 + R_5) - I_3 \left[\frac{R_3}{R_2} (R_2 + R_5) + R_5 \right] = 0$$

$$\Sigma - A I_1 - B I_3 = 0$$

$$\Sigma - C I_1 - D I_3 = 0$$

$$A = R_1 + R_4 = 3.00 \Omega$$

$$B = R_4 = 2.00 \Omega$$

$$C = \frac{R_1}{R_2} (R_2 + R_5) = 1.5 \Omega$$

$$D = \left[\frac{R_3}{R_2} (R_2 + R_5) + R_5 \right] = 2.5 \Omega$$

$$I_1 = \frac{\varepsilon - BI_3}{A} =$$

$$A\varepsilon - \frac{C\varepsilon}{A} + \frac{BC}{A}I_3 - ADI_3 = 0$$

$$(AD - BC)I_3 = \varepsilon(A - C)$$

$$I_3 = \frac{\varepsilon(A - C)}{AD - BC} = \frac{14.0 \times (1.5)}{4.5} = \frac{14.0}{3.0} = 4.7 \text{ A}$$

$$I_1 = \frac{\varepsilon}{A} - \frac{\varepsilon B}{A} \frac{(A - C)}{(AD - BC)} = \frac{14}{3} - \frac{2}{3} \times \frac{14}{3} = \frac{14}{9} \text{ A}$$

~~$\frac{7}{3} \text{ A} = 2.3 \text{ A}$~~

$$I_4 = I_1 - I_3$$

$$I_4 = \frac{14}{9} - \frac{14}{3} = -\frac{28}{9} \text{ A}$$


$$I_2 = \frac{I_1 R_1 + I_3 R_3}{R_2} = \frac{\frac{14}{9} + \frac{14}{3}}{2} = \frac{7}{9} + \frac{7}{3} = \frac{28}{9} \text{ A}$$

$$I_5 = \frac{28}{9} + \frac{14}{3} = \frac{28}{9} + \frac{42}{9} = \frac{70}{9} \text{ A}$$

$$I = \frac{42}{9} \text{ A}$$

(b) $\varepsilon = IR \Rightarrow \frac{14.0}{42} = \frac{2.0}{6} = \frac{9}{3} = 3 \Omega$

26.91

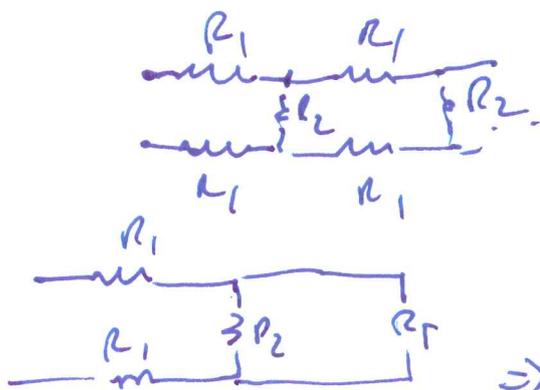

$$R_T = 2R_1 + \frac{R_2 R_T}{R_1 + R_T}$$

$$\Rightarrow R_T^2 + R_2 R_T = 2R_1 (R_2 + R_T)$$

$$R_T^2 - 2R_1 R_T - 2R_1 R_2 = 0$$

$$R_T = \frac{2R_1 \pm \sqrt{4R_1^2 + 8R_1 R_2}}{2}$$


$$= R_1 \pm \sqrt{R_1^2 + 2R_1 R_2}$$

cannot be minus since resistance cannot be negative!


8.

$$R_T = R_1 + \sqrt{R_1^2 + 2R_1 R_2}$$

24.69

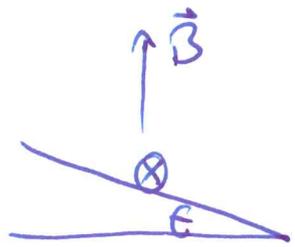

free-body diagram

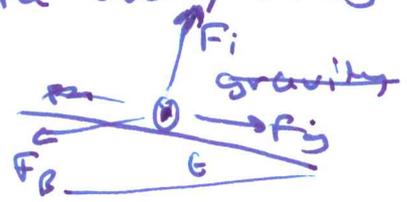

mass M

length L


$$F_B = I L B$$

$$F_B \cos \theta = F_g = M g$$

$$\Rightarrow I L B \cos \theta = M g$$


$$I = \frac{M g}{L B \cos \theta}$$

direction of current

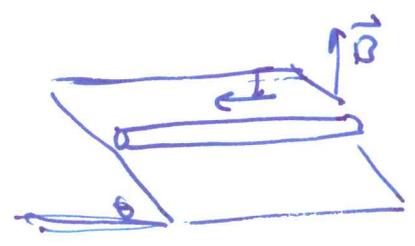

a. 24.70

14

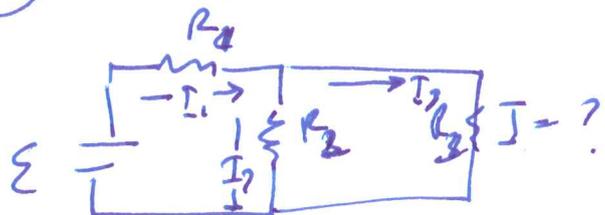

$$R_1 = 25.0 \Omega$$

$$R_2 = 10.0 \Omega$$

$$R_3 = 10.0 \Omega$$

$$\mathcal{E} = 170.0 \text{ V}$$

$$I_1 = I_2 + I_3$$

$$\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$

$$\mathcal{E} - I_1 R_1 - I_3 R_3 = 0$$

$$\mathcal{E} - I_1 R_1 - I_1 R_2 + I_3 R_2 = 0$$

$$\mathcal{E} - I_1 R_1 - I_3 R_3 = 0$$

$$\mathcal{E} - A I_1 - B I_3 = 0$$

$$A = R_1 + R_2 = 35.0 \Omega$$

$$B = -R_2 = -10.0 \Omega$$

$$\mathcal{E} - C I_1 - D I_3 = 0$$

$$C = R_1 = 25.0 \Omega$$

$$D = R_3 = 10.0 \Omega$$

$$I_1 = \frac{\mathcal{E} - D I_3}{C}$$

$$\mathcal{E} - \frac{A\mathcal{E}}{C} + \frac{AD I_3}{C} - B I_3 = 0$$

$$\mathcal{E} C - A\mathcal{E} + (AD - BC) I_3 = 0$$

$$I_3 = \frac{AD - BC}{AD - BC} \mathcal{E}$$

$$I_3 = \frac{170.0 \times 10.0}{35.0 + 25.0} = \frac{1700}{60} = 2.83 \text{ A}$$

$$|\vec{F}_B| = I \vec{L} \times \vec{B} = I L B$$

$$= 2 \times 1.50 \times 1.60 = 4.8 \text{ N}$$

$$m = \frac{2.60}{8} = \frac{2.60}{9.8} = .26$$


$$a = \frac{4.8}{.26} = 18.5 \frac{m}{s^2}$$

10.) 74.78

$$I = 15.0 A$$


$$a = .08 m$$

$$b = .06 m$$

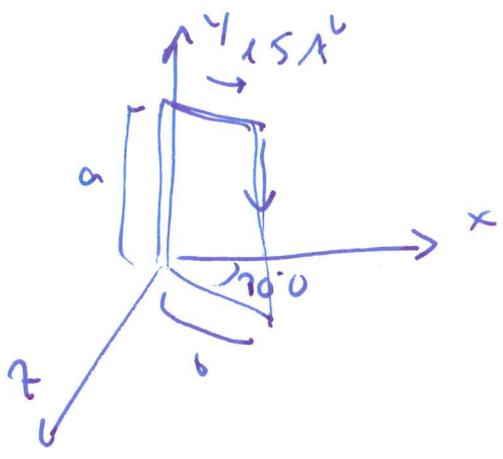

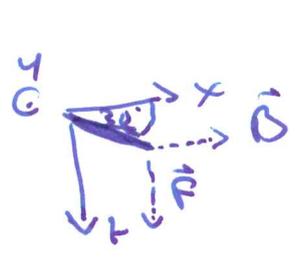(a) $B = \odot .48 T \quad \vec{B} = (.B_0, 0, 0)$

torque originates from outer vertical segment



$$\vec{F} = I \vec{L} \times \vec{B}$$

$$F = I L B = 15.0 \cdot (.08) \cdot (.48)$$


$$\vec{\tau} = \vec{r} \times \vec{F} \Rightarrow \tau = r F \sin \theta$$

$$\tau = b F \sin 60$$

$$\tau = .03 \text{ Nm}$$

direction \odot

(b) field in -z direction

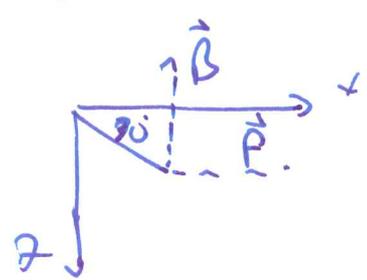

~~direction~~

$$\tau = I a B b \sin 30 = .0178 \text{ Nm}$$

direction \odot

28

(16)

11.) 28.60

$$q_1 = 4.80 \times 10^{-6} \text{ C}$$


$$\vec{r}_1 = (0, 0.250, 0)$$

$$\vec{v}_1 = 9.20 \times 10^5 \frac{\text{m}}{\text{s}} \hat{i}$$

$$q_2 = -7.90 \times 10^{-6} \text{ C}$$

$$\vec{r}_2 = (0.150 \text{ m}, 0, 0)$$

$$\vec{v}_2 = (-5.30 \times 10^5 \frac{\text{m}}{\text{s}}) \hat{j}$$

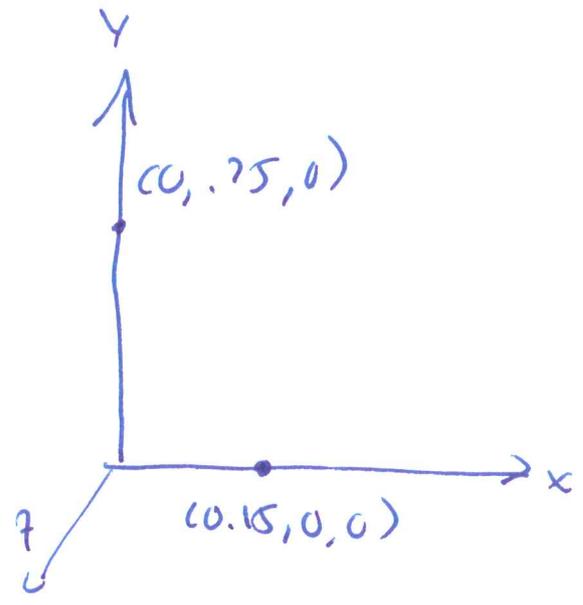force on q_2

$$\vec{F} = q_2 (\vec{E} + \vec{v}_2 \times \vec{B})$$

$$\vec{E}_1 = \frac{q_1}{4\pi\epsilon_0 r^3} (x \hat{i} + y \hat{j})$$

$$r = \sqrt{(0.15)^2 + (0.25)^2}$$

$$\vec{F}_E = \frac{q_1 q_2}{4\pi\epsilon_0 r^3} (x \hat{i} + y \hat{j})$$

electric force:

$$F_x = \frac{q_1 q_2 (0.150)}{4\pi\epsilon_0 (0.292)}$$

$$F_y = - \frac{q_1 q_2 (0.25)}{4\pi\epsilon_0 (0.292)}$$

magnetic force

need \vec{B}

$$\vec{B} = \frac{\mu_0}{4\pi} \frac{q_1 \vec{v}_1 \times \vec{r}_{21}}{r_{21}^3}$$

$$\vec{B} = \frac{q_1 \mu_0}{4\pi} \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ v_1 & 0 & 0 \\ -0.15 & -0.25 & 0 \end{vmatrix} =$$

$$\vec{B} = \frac{q_1 \mu_0}{4\pi} (-0.25) v_1 \hat{k}$$

$$\vec{F}_B = q_2 \vec{v}_2 \times \vec{B} = q_2 \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ 0 & -v_2 & 0 \\ 0 & 0 & B_z \end{vmatrix}$$

$$= q_2 (-v_2 B_z) \hat{i}$$

$$F_x = -q_2 v_2 B_z = \frac{\mu_0}{4\pi} q_1 q_2 v_2 v_1 (0.25)$$

$$F_y = 0$$

using $\frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \text{ Nm}^2/\text{C}^2$

$$\frac{\mu_0}{4\pi} = 10^{-7} \frac{\text{Tm}}{\text{A}}$$

electric: $F_x^E = -9.65 \times 10^{-3} \text{ N}$



$$F_y^E = +16.09 \times 10^{-3} \text{ N}$$

magnetic: $F_x^B = +1.69 \times 10^{-7} \text{ N}$

$$F_y^B = 0$$

12) 28.61

(a)

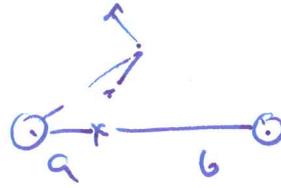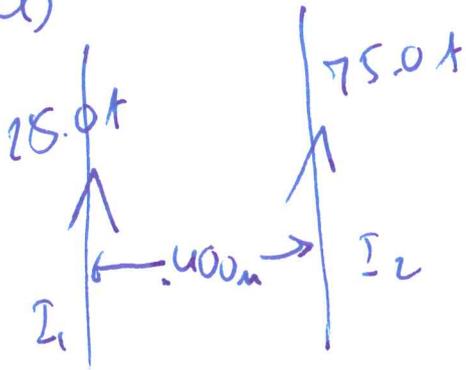

$$a + b = .400 \text{ m}$$

B-field of current 1

$$B_1 = \frac{\mu_0 I}{2\pi r} \Rightarrow \frac{25 \mu_0}{2\pi a}$$

$$\frac{25 \mu_0}{2\pi a} = \frac{75 \mu_0}{2\pi b}$$

$$B_2 = \frac{75 \mu_0}{2\pi r}$$

$$B_1 = B_2 \quad \text{if}$$

$$\frac{25 \mu_0}{2\pi a} = \frac{75 \mu_0}{2\pi b}$$


$$25b = 75a$$

$$b = 3a$$

$$a = .1 \text{ m}$$

$$b = .3 \text{ m}$$

(b)

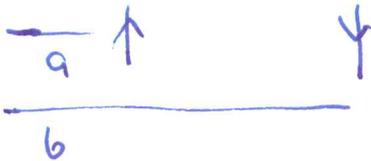

$$\frac{\mu_0 25}{4\pi a} = \frac{\mu_0 75}{4\pi b}$$


$$25b = 75a$$

$$b = 3a$$

$$a = .20 \text{ m}$$

$$b = .60 \text{ m}$$

13

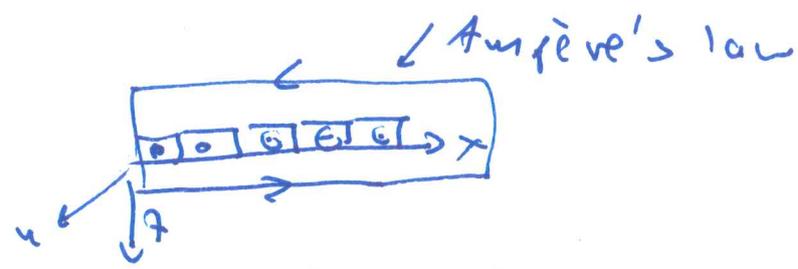


$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}}$$

below direction of \vec{B} -field \rightarrow

above direction of \vec{B} -field \leftarrow

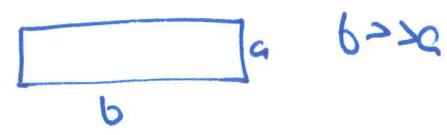take Ampère rectangle to be infinite in horizontal direction



$$\oint \vec{B} \cdot d\vec{l} = 2 B b = \mu_0 n I b$$

$$\Rightarrow B = \frac{\mu_0 n I}{2}$$