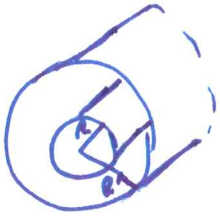


Problem Set 9: Solutions

①

1.)



energy: depends on B-field

B-field is finite in between

two shells

$$\oint \vec{B} \cdot d\vec{l} = 2\pi r B(r) = \mu_0 I$$

$$B(r) = \frac{\mu_0 I}{2\pi r}$$


energy density: $u(r) = \frac{\mu_0 I^2}{4\pi^2 r^2} \cdot 2\pi r \quad \left(= \frac{B^2(r)}{2\mu_0} \right)$

$$= \frac{\mu_0 I^2}{2\pi r}$$

$$U/L = \int_r^{r'} \frac{\mu_0 I^2}{4\pi r} dr = \frac{\mu_0 I^2}{4\pi} \int_r^{r'} \frac{dr}{r} = \frac{\mu_0 I^2}{4\pi} \ln r'/r$$

2.) self-inductance

$$N \Phi = LI$$


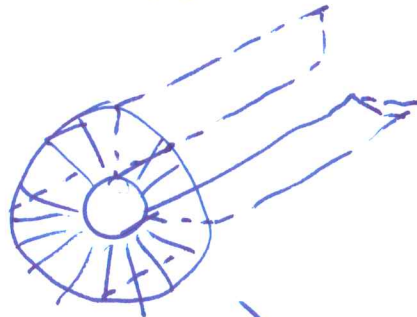


N remains constant (large $\rightarrow \infty$)

Φ increases



L decreases

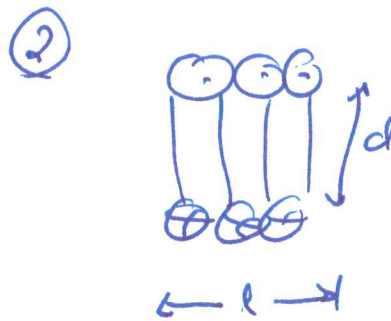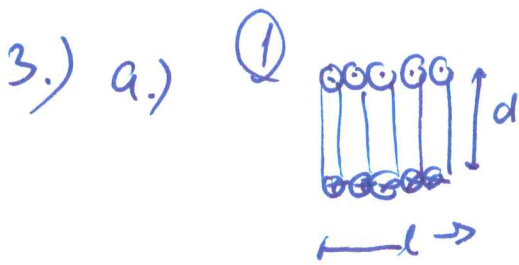

③

$$N \Phi = LI$$

$$NBA = LI$$

$$B \ell = \mu_0 NI$$

$$B = \frac{\mu_0 NI}{\ell}$$

$$\boxed{\frac{N^2 \mu_0 \pi d^2}{\ell} = L}$$

① will have larger self-inductance

b.) time constant

L

R = ?

$$R = \frac{\rho d'}{A}$$

d' - length of wire in solenoid

A - area of wire

N windings $\Rightarrow d =$

for N windings: $d' = \frac{2\pi d}{2} \cdot N = N\pi d$

$$A = \pi r^2 \Rightarrow r = \frac{\ell}{2N}$$

$$A = \frac{\pi \ell^2}{4N^2}$$

$$R = \frac{4 \rho N^3 \pi d}{\pi \ell^2}$$

time constant

$$\tau_L = \frac{L}{R} \Rightarrow \text{proportional to } \frac{1}{N}$$


larger time constant \Rightarrow fewer N

4.) series
parallel

$$L_{eq} = L_1 + L_2$$

$$V_{ab} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} \quad (3)$$

$$= (L_1 + L_2) \frac{dI}{dt}$$

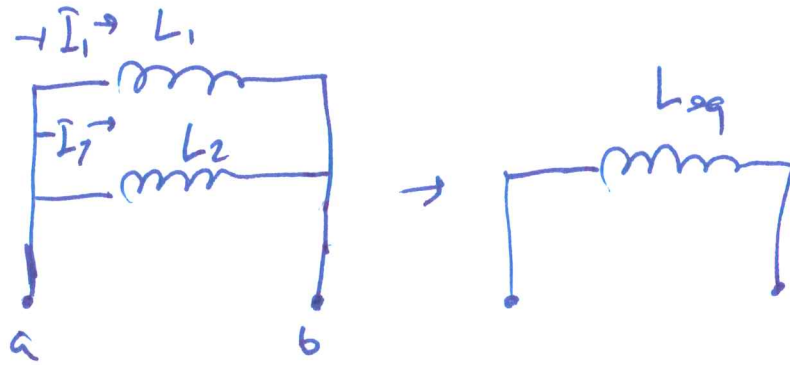

$$V_{ab} = L_{eq} \frac{dI}{dt} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} \Rightarrow \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

~~$L_{eq} = L_1$~~

$$L_{eq} \frac{dI}{dt} = L_1 \left(\frac{dI}{dt} - \frac{dI_2}{dt} \right) = L_2 \frac{dI_2}{dt}$$


$$(L_{eq} - L_1) \frac{dI}{dt} = -L_1 \frac{dI_2}{dt} = -\frac{L_1 L_{eq}}{L_2} \frac{dI}{dt}$$

$$(L_{eq} - L_1) L_2 = -L_1 L_{eq}$$

$$L_{eq} (L_1 + L_2) = L_1 L_2$$

$$\Rightarrow L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

5.) mutual inductance not negligible:

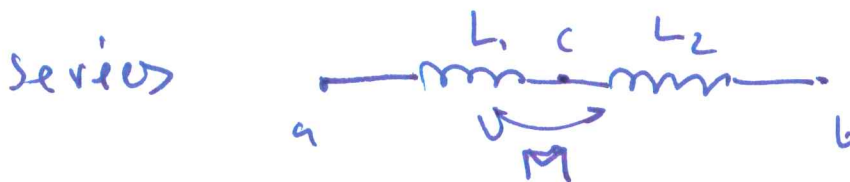


$$V_{ac} = L_1 \frac{dI}{dt} + M \frac{dI}{dt}$$

$$V_{cb} = L_2 \frac{dI}{dt} + M \frac{dI}{dt} \Rightarrow V_{ab} = (L_1 + L_2 + 2M) \frac{dI}{dt}$$

$$L_{eq} = L_1 + L_2 + 2M$$

parallel

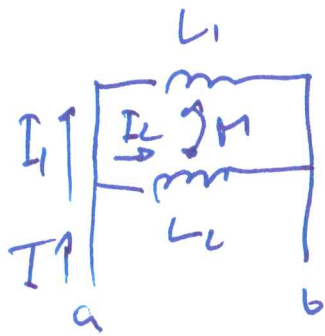

(4)

$$V_{ab} = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

$$= L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = L_{eq} \frac{dI}{dt}$$

$$\frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$L_{eq} \frac{dI}{dt} = L_1 \frac{dI_1}{dt} + M \left(\frac{dI}{dt} - \frac{dI_1}{dt} \right)$$

$$L_{eq} \frac{dI}{dt} = L_2 \left(\frac{dI}{dt} - \frac{dI_1}{dt} \right) + M \frac{dI_1}{dt}$$

$$(L_{eq} - M) \frac{dI}{dt} = (L_1 - M) \frac{dI_1}{dt}$$

$$(L_{eq} - L_2) \frac{dI}{dt} = (M - L_2) \frac{dI_1}{dt}$$


$$\Rightarrow (L_{eq} - M) = \frac{(L_1 - M)(L_{eq} - L_2)}{(M - L_2)}$$

$$(M - L_2)(L_{eq} - M) = (L_1 - M)(L_{eq} - L_2)$$

$$L_{eq}(M - L_2) - M(M - L_2) = L_{eq}(L_1 - M) - L_2(L_1 - M)$$

$$L_{eq}(2M - L_2 - L_1) = M(M - L_2) - L_2(L_1 - M)$$

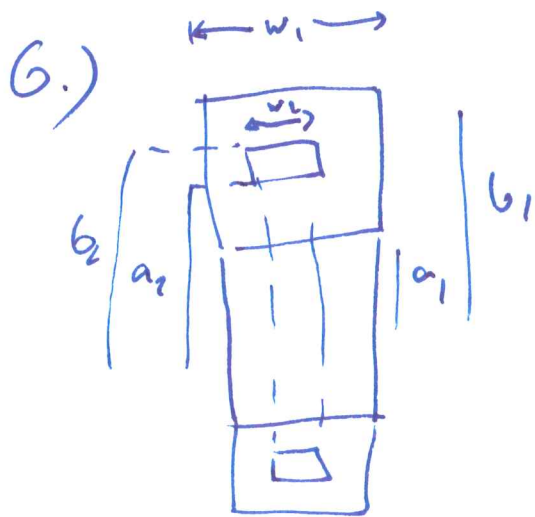
$$L_{eq} = \frac{M^2 - L_1 L_2}{2M - L_1 - L_2}$$



N_2, N_1

Ⓟ

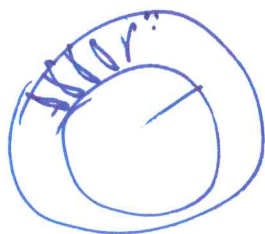magnetic field inside rectangular toroidal solenoid



~~$\oint \vec{B} \cdot d\vec{r} =$~~

$$\oint \vec{B} \cdot d\vec{r} = \mu_0 N I$$

$$B(r) = \frac{\mu_0 N I}{2\pi r}$$

inductance of solenoid 1

$$N_1 \Phi = L_1 I \quad \Phi = w_1 \int_{a_1}^{b_1} \frac{\mu_0 N_1 I}{2\pi r} dr = \frac{\mu_0 N_1 w_1 I}{2\pi} \ln b_1/a_1$$

$$L_1 = \frac{N_1^2 \mu_0 w_1}{2\pi} \ln b_1/a_1$$

inductance of solenoid 2:

$$L_2 = \frac{N_2^2 \mu_0 w_2}{2\pi} \ln b_2/a_2$$

mutual inductance: $N_1 \Phi_2 = M I_2$

$$\frac{N_2 N_1 \mu_0 w_2 \ln b_2/a_2}{2\pi}$$

for serial connection: field inside adds in a simple way

for example: inductance in solenoid 1 due to current 1

$$\begin{aligned} N_1 \Phi &= N_1 (\Phi_{11} + \Phi_{12}) = L_1 I + \underbrace{N_1 \Phi_{12}}_{\text{flux in 1 due to current 2}} \\ &= N_1 \left(\frac{\mu_0 N_1 w_1 \ln b_1/a_1}{2\pi} I + \frac{\mu_0 N_2 w_2 \ln b_2/a_2}{2\pi} I \right) \\ &= (L_1 + M) I \end{aligned}$$

inductance in solenoid 2

(6)

$$N_2(\Phi_{22} + \Phi_{21}) = ? \quad \Phi_{22} - \text{flux in 2 due to current in 2}$$

$$\Phi_{21} - \text{flux in 2 due to current in 1}$$

$$N_2 \frac{N_2 \mu_0 w_2 (\ln b_2 / a_2) I}{2\pi} + N_2 \frac{N_1 \mu_0 w_2 (\ln b_2 / a_2) I}{2\pi}$$


$$= (L_2 + M) I$$

parallel connection:

$$N_1(\Phi_{11} + \Phi_{12}) = \frac{N_1 \mu_0 N_1 w_1 (\ln b_1 / a_1) I_1}{2\pi} + \frac{N_1 \mu_0 N_2 w_2 (\ln b_2 / a_2) I_2}{2\pi}$$

$$= L_1 I_1 + M I_2$$
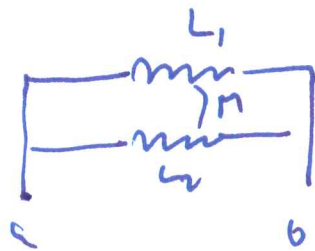
$$N_2(\Phi_{22} + \Phi_{21}) = L_2 I_2 + M I_1$$



$$\rightarrow V_{ab} = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$


$$= L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = L_{eq} \frac{dI}{dt}$$

$$I = I_1 + I_2$$

- subsequently derivation is the same as in problem 5

7.) sheet:

7

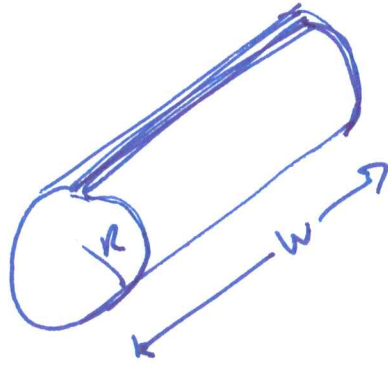

inductance
 $N\Phi = LI$

$\Phi = ?$


$B \cdot w = \mu_0 I$

$B = \frac{\mu_0 I}{w}$

flux = $\frac{\mu_0 I}{w} \pi R^2$

$L = \frac{\mu_0 \pi R^2}{w}$

8.)

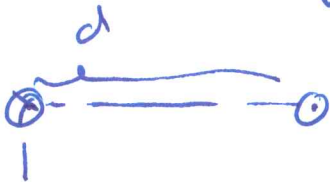

$B(r) \cdot 2\pi r = \mu_0 I$

assume length L


$B(r) = \frac{\mu_0 I}{2\pi r}$

$\Phi = 2L \int_{a/2}^{d-a/2} dr \frac{\mu_0 I}{2\pi r} = \frac{2L\mu_0 I}{2\pi} \ln \frac{d-a/2}{a/2} = \frac{L\mu_0 I}{\pi} \ln \left(\frac{2d-a}{a} \right)$

$\Phi = LI \Rightarrow L = \frac{\mu_0 I}{\pi} \ln \left(\frac{2d-a}{a} \right)$

inductance per unit length $\frac{L}{l} = \frac{\mu_0 I}{\pi} \ln \left(\frac{2d-a}{a} \right)$

9.)

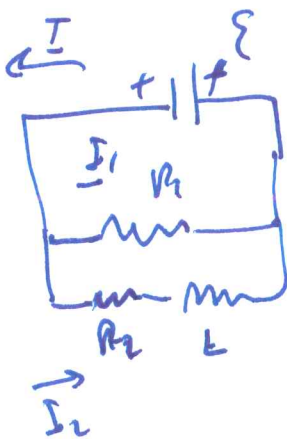

$I = I_1 + I_2$

$E - I_1 R_1 = 0$

$E - I_2 R_2 - L \frac{dI_2}{dt} = 0$


$\frac{E}{R_2} - I_2 - \frac{L}{R_2} \frac{dI_2}{dt} = 0$

~~$\frac{E - I_1 R_1}{R_2} = \frac{L}{R_2} \frac{dI_2}{dt}$~~

~~$\frac{L}{L} = \frac{dI_2}{E/R_2 - I_2}$~~

answers to questions: (a) ϵ (b) a (c) ϵ (d) c (8)

open switch: only one loop

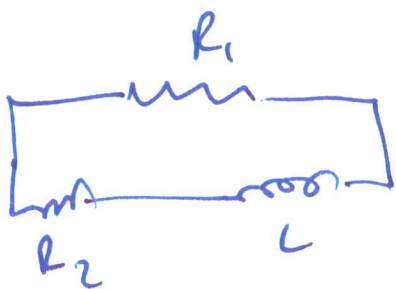

$$I(0) = \epsilon / R_2$$

$$-I R_1 - L \frac{dI}{dt} - I R_2 = 0$$

$$-I (R_1 + R_2) - L \frac{dI}{dt} = 0$$

$$-I R - L \frac{dI}{dt} = 0$$

$$I(t) = \frac{\epsilon}{R_2} e^{-\frac{tL}{R_1+R_2}} e^{-\frac{t(R_1+R_2)}{L}}$$

answers to questions:

(e) $-\frac{\epsilon R_1}{R_2}$ (f) b (g) $\frac{\epsilon (R_1 + R_2)}{R_2}$ (h) d

10.) assume coil is shorter

$$N' < N$$

mutual inductance $N' \Phi = M I$

$$\Phi = B A R^2$$

~~$$B L^2 = \mu_0 N' I$$~~

$$B = \frac{\mu_0 N I}{L}$$

$$M = \frac{\mu' N \mu_0}{L}$$

11.) current is I $V = I R$ $\frac{d\phi}{dt} = R$ $E = \frac{I \phi}{A}$

$$E_{ed} = J A R$$


$$E = \frac{J A R}{a} = J \phi$$

energy density electric: $\frac{E^2}{2\epsilon_0} = \frac{J^2 \phi^2}{2\epsilon_0 a^2}$

energy density magnetic: $\frac{B^2}{2\mu_0} = \frac{\mu_0^2 I^2}{8\pi^2 a^2 \mu_0} = \frac{\mu_0 I^2}{8\pi^2 a}$

$$B = \frac{\mu_0 I}{2\pi a}$$

12.)

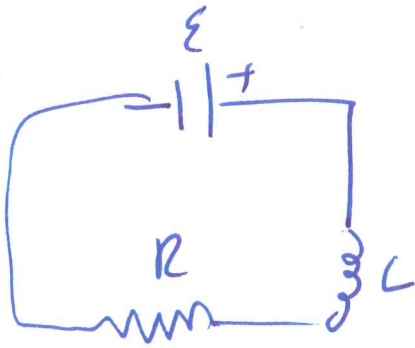

(9)

$$\varepsilon - L \frac{dI}{dt} - IR = 0$$

current:

$$\varepsilon - IR = L \frac{dI}{dt}$$

$$\frac{\varepsilon}{R} - I = \frac{L}{R} \frac{dI}{dt}$$

$$\frac{1}{\frac{\varepsilon}{R} - I} = \frac{dt}{dI} \frac{R}{L}$$

$$\frac{dI}{\frac{\varepsilon}{R} - I} = dt \left(\frac{R}{L} \right)$$

$$\frac{dI}{I - \varepsilon/R} = - dt \left(\frac{R}{L} \right)$$

$$\ln \frac{I - \varepsilon/R}{-\varepsilon/R} = -t \left(\frac{R}{L} \right) \Rightarrow \frac{I - \varepsilon/R}{-\varepsilon/R} = e^{-tR/L}$$

$$I(t) = \frac{\varepsilon}{R} (1 - e^{-tR/L})$$

energy stored in inductor $\frac{LI^2}{2}$

$$L \frac{\varepsilon^2}{R^2} (1 - e^{-tR/L})^2$$